

实验十一 RV32I 单周期 CPU

姓名：徐沐杰

学号：211240088

班级：1班

邮箱：litrehinn@smail.nju.edu.cn



实验时间：2022.12.9


实验十一 RV32I 单周期 CPU

1.实验目的

利用 FPGA 实现 RV32I 指令集中除系统控制指令之外的其余指令。利用单周期方式实现 RV32I 的控制通路及数据通路，并能够顺利通过功能仿真。

2.实验原理

 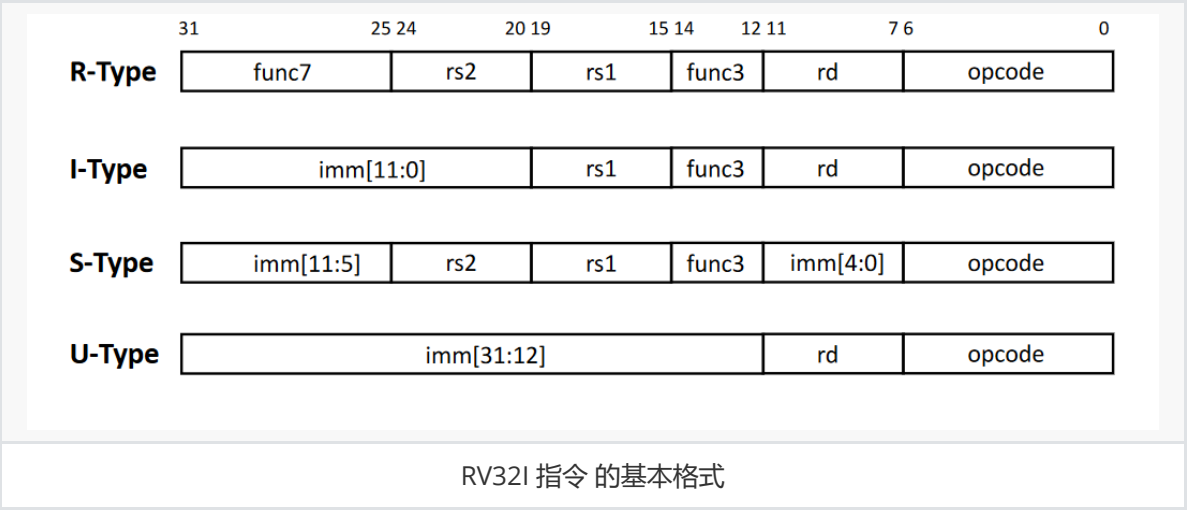

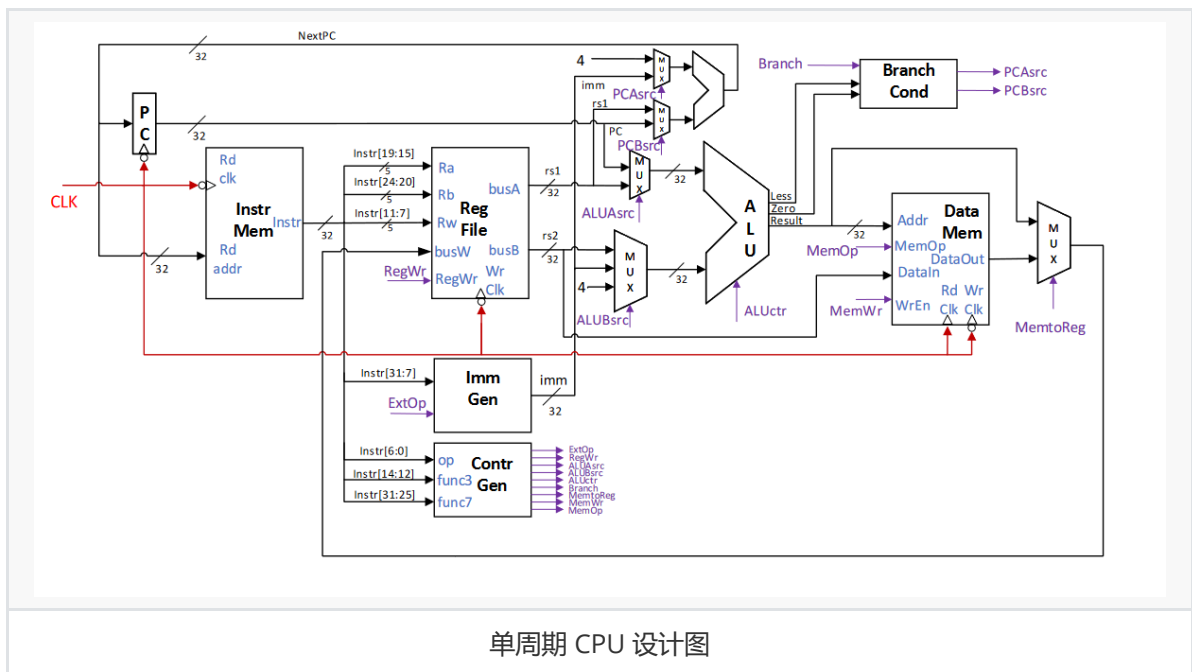

3.实验环境/器材

在线仿真测试平台。

4.程序代码或流程图

oj 通关代码

```
module control_signal_generator (
    input wire [31:0] instr,
    output wire [2:0] ExtOp,
    output wire      RegWr,
    output wire      ALUSrc,
    output wire [1:0] ALUBsrc,
    output wire [3:0] ALUctr,
    output wire [2:0] Branch,
    output wire      MemtoReg,
    output wire      MemWr,
    output wire [2:0] MemOp,
    output wire [(5)-1:0] rd,
    output wire [(5)-1:0] rs1,
    output wire [(5)-1:0] rs2
);
// ===== Decode =====
wire [6:0] op    = instr[6:0];
assign rs1  = instr[19:15];
assign rs2  = instr[24:20];
assign rd   = instr[11:7];
wire [2:0] func3 = instr[14:12];
wire [6:0] func7 = instr[31:25];
// =====

reg [18:0] control_signal;
assign {ExtOp, RegWr, Branch, MemtoReg, MemWr, MemOp, ALUSrc, ALUBsrc,
ALUctr} = control_signal;

always @(*) begin
```

```

    case {op[6:2], func3, func7[5]}
        //ARI
        9'b01101xxxx: control_signal = 19'b001_1_000_0_0_000_0_01_0011;
        9'b00101xxxx: control_signal = 19'b001_1_000_0_0_000_1_01_0000;
        9'b00100000x: control_signal = 19'b000_1_000_0_0_000_0_01_0000;
        9'b00100010x: control_signal = 19'b000_1_000_0_0_000_0_01_0010;
        9'b00100011x: control_signal = 19'b000_1_000_0_0_000_0_01_1010;
        9'b00100100x: control_signal = 19'b000_1_000_0_0_000_0_01_0100;
        9'b00100110x: control_signal = 19'b000_1_000_0_0_000_0_01_0110;
        9'b00100111x: control_signal = 19'b000_1_000_0_0_000_0_01_0111;
        9'b001000010: control_signal = 19'b000_1_000_0_0_000_0_01_0001;
        9'b001001010: control_signal = 19'b000_1_000_0_0_000_0_01_0101;
        9'b001001011: control_signal = 19'b000_1_000_0_0_000_0_01_1101;
        9'b011000000: control_signal = 19'b000_1_000_0_0_000_0_00_0000;
        9'b011000001: control_signal = 19'b000_1_000_0_0_000_0_00_1000;
        9'b011000010: control_signal = 19'b000_1_000_0_0_000_0_00_0001;
        9'b011000100: control_signal = 19'b000_1_000_0_0_000_0_00_0010;
        9'b011000110: control_signal = 19'b000_1_000_0_0_000_0_00_1010;
        9'b011001000: control_signal = 19'b000_1_000_0_0_000_0_00_0100;
        9'b011001010: control_signal = 19'b000_1_000_0_0_000_0_00_0101;
        9'b011001011: control_signal = 19'b000_1_000_0_0_000_0_00_1101;
        9'b011001100: control_signal = 19'b000_1_000_0_0_000_0_00_0110;
        9'b011001110: control_signal = 19'b000_1_000_0_0_000_0_00_0111;
        //J
        9'b11011xxxx: control_signal = 19'b100_1_001_0_0_000_1_10_0000;
        9'b11001000x: control_signal = 19'b000_1_010_0_0_000_1_10_0000;
        9'b11000000x: control_signal = 19'b011_0_100_0_0_000_0_00_0010;
        9'b11000001x: control_signal = 19'b011_0_101_0_0_000_0_00_0010;
        9'b11000100x: control_signal = 19'b011_0_110_0_0_000_0_00_0010;
        9'b11000101x: control_signal = 19'b011_0_111_0_0_000_0_00_0010;
        9'b11000110x: control_signal = 19'b011_0_110_0_0_000_0_00_1010;
        9'b11000111x: control_signal = 19'b011_0_111_0_0_000_0_00_1010;
        //L&S
        9'b00000000x: control_signal = 19'b000_1_000_1_0_000_0_01_0000;
        9'b00000001x: control_signal = 19'b000_1_000_1_0_001_0_01_0000;
        9'b00000010x: control_signal = 19'b000_1_000_1_0_010_0_01_0000;
        9'b00000100x: control_signal = 19'b000_1_000_1_0_100_0_01_0000;
        9'b00000101x: control_signal = 19'b000_1_000_1_0_101_0_01_0000;
        9'b01000000x: control_signal = 19'b010_0_000_0_1_000_0_01_0000;
        9'b01000001x: control_signal = 19'b010_0_000_0_1_001_0_01_0000;
        9'b01000010x: control_signal = 19'b010_0_000_0_1_010_0_01_0000;
        default: begin control_signal = 19'b010_0_000_0_1_010_0_01_0000; end
    endcase
end

endmodule

module imm_generator (
    input wire [31:0] instr,
    input wire [2:0] ExtOp,
    output reg [31:0] imm
);
    always @(*)
        case (ExtOp)
            3'b000: imm = {{20{instr[31]}}}, instr[31:20]]; //I
            3'b001: imm = {instr[31:12], 12'b0}; //U
            3'b010: imm = {{20{instr[31]}}}, instr[31:25], instr[11:7]]; //S

```

```

        3'b011: imm = {{20{instr[31]}}}, instr[7], instr[30:25], instr[11:8],
1'b0}; //B
        3'b100: imm = {{12{instr[31]}}}, instr[19:12], instr[20], instr[30:21],
1'b0}; //J
    endcase
endmodule

module pc_generator(
    input  wire    [(32)-1:0]    pc,           //pcbsrc
    input  wire    pc_source_sel, //pcasrc
    input  wire    pc_offset_sel,
    input  wire    [(32)-1:0]    jalr_reg,
    input  wire    [(32)-1:0]    offset,
    output wire    [(32)-1:0]    next_pc
);

    wire [(32)-1:0] pc_source = pc_source_sel ? jalr_reg : pc;
    wire [(32)-1:0] pc_offset = pc_offset_sel ? offset : 4;

    assign next_pc = pc_source + pc_offset;

endmodule

module inst_memory (
    input  wire clk,
    input  wire [31:0] addr,
    output reg [31:0] instr
);
    parameter instr_size = 1000;
    reg [31:0] instr_mem [instr_size:0];
    initial
    begin
        $readmemh("", instr_mem);
    end
    always @(negedge clk)
        instr <= instr_mem[addr];
endmodule

module data_memory(
    input  [31:0] addr,
    output reg [31:0] dataout,
    input  [31:0] datain,
    input  rdclk,
    input  wrclk,
    input  [2:0] memop,
    input  we
);
    //add your code here
    wire [31:0] unit;
    wire [1:0] offset;
    wire [31:0] data;
    reg [31:0] mem [1000:0];
    assign unit = addr / 4;
    assign offset = addr % 4;
    assign data = mem[unit];
    integer i;
    always @(posedge rdclk)

```

```

begin
  if(we == 1'b0)
    begin
      case(memop)
        3'b000:
          begin
            if(data[offset * 8 + 7] == 1'b1)
              dataout[31:8] = {24{1'b1}};
            else
              dataout[31:8] = {24{1'b0}};
            case(offset)
              2'b00: dataout[7:0] = data[7:0];
              2'b01: dataout[7:0] = data[15:8];
              2'b10: dataout[7:0] = data[23:16];
              2'b11: dataout[7:0] = data[31:24];
            endcase
          end
        3'b001:
          begin
            if(data[offset * 8 + 15] == 1'b1)
              dataout[31:16] = {16{1'b1}};
            else
              dataout[31:16] = {16{1'b0}};
            case(offset)
              2'b00: dataout[15:0] = data[15:0];
              2'b10: dataout[15:0] = data[31:16];
            endcase
          end
        3'b010:
          begin
            dataout[31:0] = data;
          end
        3'b100:
          begin
            dataout[31:8] = {24{1'b0}};
            case(offset)
              2'b00: dataout[7:0] = data[7:0];
              2'b01: dataout[7:0] = data[15:8];
              2'b10: dataout[7:0] = data[23:16];
              2'b11: dataout[7:0] = data[31:24];
            endcase
          end
        3'b101:
          begin
            dataout[31:16] = {16{1'b0}};
            case(offset)
              2'b00: dataout[15:0] = data[15:0];
              2'b10: dataout[15:0] = data[31:16];
            endcase
          end
      endcase
    end
  end
  always @(posedge wrclk)
    begin
      if(we == 1'b1)
        begin
          case(memop)

```

```

        3'b000:
            begin
                case(offset)
                    2'b00: mem[unit][7:0] = datain[7:0];
                    2'b01: mem[unit][15:8] = datain[7:0];
                    2'b10: mem[unit][23:16] = datain[7:0];
                    2'b11: mem[unit][31:24] = datain[7:0];
                endcase
            end
        3'b001:
            begin
                case(offset)
                    2'b00: mem[unit][15:0] = datain[15:0];
                    2'b10: mem[unit][31:16] = datain[15:0];
                endcase
            end
        3'b010:
            begin
                mem[unit][31:0] = datain[31:0];
            end
        endcase
    end
end
endmodule

```

```

module regheap (
    input wire wrClk,
    input wire [4:0] Ra,
    input wire [4:0] Rb,
    input wire [4:0] Rw,
    input wire RegWr,
    input wire [31:0] busW,
    output wire [31:0] busA,
    output wire [31:0] busB
);
    integer i;

    reg [31:0] regs [31:0];
    initial begin
        for (i = 0; i < 32; i = i + 1)
            regs[i] = 0;
        end
    assign busA = regs[Ra];
    assign busB = regs[Rb];
    always @(negedge wrClk)
    begin
        if(RegWr && Rw)
            regs[Rw] <= busW;
        end
    endmodule

```

```

module ALU(
    input [31:0] dataa,
    input [31:0] datab,
    input [3:0] ALUctr,
    output reg less,
    output reg zero,

```

```

        output reg [31:0] aluresult
    );
    //add your code here
    reg [31:0] reverse;
    reg [31:0] temp;
    reg carry;
    reg of;
    wire [4:0] offset;
    assign offset = datab[4:0];
    always @(*)
    begin
        case(ALUctr[2:0])
            3'b000:
                begin
                    if(ALUctr[3] == 1'b0)
                        begin
                            {carry, aluresult} = dataa + datab;
                            zero = (!aluresult);
                        end
                    else
                        begin
                            {carry, aluresult} = dataa + ~datab + 1;
                            zero = (!aluresult);
                        end
                    end
                end
            3'b001:
                begin
                    aluresult = dataa << datab[4:0];
                    zero = (!aluresult);
                end
            3'b010:
                begin
                    if(ALUctr[3] == 1'b0)
                        begin
                            reverse = ~datab;
                            {carry, aluresult} = dataa + reverse + 1;
                            of = (dataa[31] == reverse[31]) && (aluresult [31] !=
dataa[31]);
                            less = (aluresult[31] ^ of) ? 1'b1 : 1'b0;
                            aluresult = less;
                        end
                    else
                        begin
                            reverse = ~datab;
                            {carry, aluresult} = dataa + reverse + 1;
                            less = (carry ^ 1) ? 1'b1 : 1'b0;
                            aluresult = less;
                        end
                    end
                    zero = (dataa == datab);
                end
            3'b011:
                begin
                    aluresult = datab;
                    zero = (!aluresult);
                end
            3'b100:
                begin
                    aluresult = dataa ^ datab;

```



```

        zero = (!alurest);
    end
3'b101:
    begin
        if(ALUctr[3] == 1'b0)
            begin
                temp = offset[0] ? {32'b0, dataa[31:1]} : dataa;
                temp = offset[1] ? {32'b0, temp[31:2]} : temp;
                temp = offset[2] ? {32'b0, temp[31:4]} : temp;
                temp = offset[3] ? {32'b0, temp[31:8]} : temp;
                temp = offset[4] ? {32'b0, temp[31:16]} : temp;
            end
        else
            begin
                temp = offset[0] ? {dataa[31], dataa[31:1]} : dataa;
                temp = offset[1] ? {{2{temp[31]}}, temp[31:2]} : temp;
                temp = offset[2] ? {{4{temp[31]}}, temp[31:4]} : temp;
                temp = offset[3] ? {{8{temp[31]}}, temp[31:8]} : temp;
                temp = offset[4] ? {{16{temp[31]}}, temp[31:16]} : temp;
            end
        alurest = temp;
        zero = (!alurest);
    end
3'b110:
    begin
        alurest = dataa | datab;
        zero = (!alurest);
    end
3'b111:
    begin
        alurest = dataa & datab;
        zero = (!alurest);
    end
endcase
end
endmodule

module jump_control(
    input  wire  [2:0]  branch,
    input  wire      zero,
    input  wire      less,
    output wire      pc_source_sel,
    output wire      pc_offset_sel
);

    reg [1:0] pc_sel;
    assign {pc_source_sel, pc_offset_sel} = pc_sel;

    always @(*)
        casex ({branch, zero, less})
            5'b000xx: pc_sel = 2'b00;
            5'b001xx: pc_sel = 2'b01;
            5'b010xx: pc_sel = 2'b11;
            5'b1000x: pc_sel = 2'b00;
            5'b1001x: pc_sel = 2'b01;
            5'b1010x: pc_sel = 2'b01;
            5'b1011x: pc_sel = 2'b00;
            //to-do

```

```

        5'b110x0: pc_sel = 2'b00;
        5'b110x1: pc_sel = 2'b01;
        5'b111x0: pc_sel = 2'b01;
        5'b111x1: pc_sel = 2'b00;
    endcase

endmodule

module CPU(
    input  wire      clk,
    input  wire      rst,
    output wire  [(32)-1:0] inst_read_addr,
    input  wire  [(32)-1:0] inst_read_data,
    output wire      inst_read_en,
    output wire  [(32)-1:0] data_read_addr,
    output wire  [(32)-1:0] data_write_addr,
    input  wire  [(32)-1:0] data_read_data,
    output wire  [(32)-1:0] data_write_data,
    output wire      data_read_en,
    output wire      data_write_en,
    output wire  [2:0]    data_mode
);

    reg [(32)-1:0] pc;
    wire [(32)-1:0] next_pc, jalr_reg, offset;
    wire pc_offset_sel, pc_source_sel;
    wire [(32)-1:0] inst = inst_read_data;
    wire RegWr, ALUASrc, MemtoReg, MemWr;
    wire [2:0] Branch, MemOp, ExtOp;
    wire [1:0] ALUBsrc;
    wire [3:0] ALUctr;
    wire [(5)-1:0] Ranum, Rbnum, Rwnum;
    wire [(32)-1:0] Ra, Rb;
    wire [(32)-1:0] imm;

    pc_generator PG (
        .next_pc(next_pc),
        .pc_offset_sel(pc_offset_sel),
        .pc_source_sel(pc_source_sel),
        .pc(pc),
        .jalr_reg(Ra),
        .offset(imm)
    );

    always @(negedge clk, posedge rst)
        if (rst) pc <= 0;
        else pc <= next_pc;

    assign inst_read_addr = next_pc;

    control_signal_generator CSG(
        .instr(inst),
        .ALUASrc(ALUASrc),
        .ALUBsrc(ALUBsrc),
        .ALUctr(ALUctr),
        .Branch(Branch),
        .MemtoReg(MemtoReg),
        .MemWr(MemWr),

```

```

        .MemOp(MemOp),
        .ExtOp(ExtOp),
        .RegWr(RegWr),
        .rs1(Ranum),
        .rs2(Rbnum),
        .rd(Rwnum)
    );

    imm_generator IG(
        .instr(inst),
        .ExtOp(ExtOp),
        .imm(imm)
    );

    wire [(32)-1:0] aluresult;

    wire [(32)-1:0] dataa = ALUAsrc ? pc : Ra;
    reg [(32)-1:0] datab;

    regheap RH(
        .wrClk(clk),
        .RegWr(RegWr),
        .Ra(Ranum),
        .Rb(Rbnum),
        .Rw(Rwnum),
        .busW(MemtoReg ? data_read_data : aluresult),
        .busA(Ra),
        .busB(Rb)
    );

    always @(*)
        case (ALUBsrc)
            2'b01: datab = imm;
            2'b10: datab = 4;
            2'b00: datab = Rb;
        endcase

    wire less, zero;

    ALU alu(
        .dataa(dataa),
        .datab(datab),
        .ALUctr(ALUctr),
        .less(less),
        .zero(zero),
        .aluresult(aluresult)
    );

    jump_control JC(
        .branch(Branch),
        .less(less),
        .zero(zero),
        .pc_offset_sel(pc_offset_sel),
        .pc_source_sel(pc_source_sel)
    );

    assign data_write_en = MemWr;
    assign data_read_en = MemtoReg;

```

```

    assign inst_read_en = 1;

    assign data_mode = MemOp;
    assign data_write_addr = aluresult;
    assign data_write_data = Rb;

endmodule

module rv32is(
    input    clock,
    input    reset,
    output [31:0] imemaddr,
    input  [31:0] imemdataout,
    output  imemclk,
    output [31:0] dmemaddr,
    input  [31:0] dmemdataout,
    output [31:0] dmemdatain,
    output  dmemrdclk,
    output  dmemwrclk,
    output [2:0] dmemop,
    output  dmemwe,
    output [31:0] dbgdata
);

    assign imemclk    = ~clock;
    assign dmemrdclk = clock;
    assign dmemwrclk = ~clock;

    wire clk = clock;
    wire rst = reset;
    wire [31:0] inst_read_data = imemdataout, data_read_data = dmemdataout;
    wire [31:0] inst_read_addr, data_read_addr, data_write_addr,
data_write_data;
    reg [31:0] pc = 0;
    wire data_write_en;
    wire [2:0] data_mode;

    wire [(32)-1:0] wire_next_pc, jalr_reg, offset;
    wire pc_offset_sel, pc_source_sel;
    wire [(32)-1:0] inst = inst_read_data;
    wire RegWr, ALUASrc, MemtoReg, MemWr;
    wire [2:0] Branch, MemOp, ExtOp;
    wire [1:0] ALUBsrc;
    wire [3:0] ALUctr;
    wire [(5)-1:0] Ranum, Rbnum, Rwnum;
    wire [(32)-1:0] Ra, Rb;
    wire [(32)-1:0] imm;

    wire [(32)-1:0] next_pc;

    pc_generator PG (
        .next_pc(wire_next_pc),
        .pc_offset_sel(pc_offset_sel),
        .pc_source_sel(pc_source_sel),
        .pc(pc),
        .jalr_reg(Ra),

```

```

        .offset(imm)
    );

    assign next_pc = rst ? 0 : wire_next_pc;

    always @(negedge clk, posedge rst)
        if (rst) pc <= 0;
        else pc <= next_pc;

    assign inst_read_addr = next_pc;

    control_signal_generator CSG(
        .instr(inst),
        .ALUAsrc(ALUAsrc),
        .ALUBsrc(ALUBsrc),
        .ALUctr(ALUctr),
        .Branch(Branch),
        .MemtoReg(MemtoReg),
        .MemWr(MemWr),
        .MemOp(MemOp),
        .ExtOp(ExtOp),
        .RegWr(RegWr),
        .rs1(Ranum),
        .rs2(Rbnum),
        .rd(Rwnum)
    );

    imm_generator IG(
        .instr(inst),
        .ExtOp(ExtOp),
        .imm(imm)
    );

    wire [(32)-1:0] aluresult;

    wire [(32)-1:0] dataa = ALUAsrc ? pc : Ra;
    reg [(32)-1:0] datab;

    regheap myregfile(
        .wrClk(clk),
        .RegWr(RegWr),
        .Ra(Ranum),
        .Rb(Rbnum),
        .Rw(Rwnum),
        .busW(MemtoReg ? data_read_data : aluresult),
        .busA(Ra),
        .busB(Rb)
    );

    always @(*)
        case (ALUBsrc)
            2'b01: datab = imm;
            2'b10: datab = 4;
            2'b00: datab = Rb;
        endcase

    wire less, zero;

```

```

ALU alu(
    .dataa(dataa),
    .datab(datab),
    .ALUctr(ALUctr),
    .less(less),
    .zero(zero),
    .alurest(alurest)
);

jump_control JC(
    .branch(Branch),
    .less(less),
    .zero(zero),
    .pc_offset_sel(pc_offset_sel),
    .pc_source_sel(pc_source_sel)
);

assign data_write_en = MemWr;

assign data_mode = MemOp;
assign data_read_addr = alurest;
assign data_write_addr = alurest;
assign data_write_data = Rb;

assign dmemwe = data_write_en;
assign dmemop = data_mode;
assign dbgdata = pc;
assign imemaddr = inst_read_addr;
assign dmemaddr = MemWr ? data_write_addr : data_read_addr;
assign dmemdatain = data_write_data;
endmodule

```

5.实验步骤/过程

在本地分模块编写代码，用仿真编译器预编译命令编译合成后进行在线仿真测试。

6.测试方法

在线仿真测试。

7.实验结果

我通过了在线仿真测试。

测试结果

1/1 全部通过

测试集1

消耗内存11.22MB 代码执行时长: 0.06秒

—— 预期输出 ——

—— 实际输出 ——

~~~ Begin test case      add ~~~  
~~~ OK: end of cycle    1 reg 06 need to be 00000064, get 00000064  
~~~ OK: end of cycle    1 PC/dbgdata need to be 00000004, get 00000004  
~~~ OK: end of cycle    2 reg 07 need to be 00000014, get 00000014  
~~~ OK: end of cycle    2 PC/dbgdata need to be 00000008, get 00000008  
~~~ OK: end of cycle    3 reg 1c need to be 00000078, get 00000078  
~~~ Begin test case      alu ~~~  
~~~ OK: end of cycle    1 reg 06 need to be 0000004f, get 0000004f  
~~~ OK: end of cycle    2 reg 07 need to be 00000003, get 00000003  
~~~ OK: end of cycle    3 reg 1c need to be 0000004c, get 0000004c  
~~~ OK: end of cycle    4 reg 1c need to be 00000003, get 00000003  
~~~ OK: end of cycle    5 reg 1c need to be 00000278, get 00000278  
~~~ OK: end of cycle    6 reg 1c need to be 00000000, get 00000000  
~~~ OK: end of cycle    7 reg 1c need to be 00000001, get 00000001  
~~~ OK: end of cycle    8 reg 1c need to be 0000004c, get 0000004c  
~~~ OK: end of cycle    9 reg 1c need to be 00000009, get 00000009  
~~~ OK: end of cycle    10 reg 1c need to be 0000004f, get 0000004f  
~~~ OK: end of cycle    11 reg 06 need to be ffffffff1, get ffffffff1  
~~~ OK: end of cycle    12 reg 1c need to be ffffffff4, get ffffffff4  
~~~ OK: end of cycle    13 reg 1c need to be ffffffff6, get ffffffff6  
~~~ OK: end of cycle    14 reg 1c need to be 1fffffff6, get 1fffffff6  
~~~ OK: end of cycle    15 reg 1c need to be 00000001, get 00000001  
~~~ OK: end of cycle    16 reg 1c need to be 00000000, get 00000000  
~~~ Begin test case      mem ~~~  
~~~ OK: end of cycle    1 reg 0a need to be 00008000, get 00008000  
~~~ OK: end of cycle    2 reg 0a need to be 00008010, get 00008010

~~~ Begin test case      add ~~~  
~~~ OK: end of cycle    1 reg 06 need to be 00000064, get 00000064  
~~~ OK: end of cycle    1 PC/dbgdata need to be 00000004, get 00000004  
~~~ OK: end of cycle    2 reg 07 need to be 00000014, get 00000014  
~~~ OK: end of cycle    2 PC/dbgdata need to be 00000008, get 00000008  
~~~ OK: end of cycle    3 reg 1c need to be 00000078, get 00000078  
~~~ Begin test case      alu ~~~  
~~~ OK: end of cycle    1 reg 06 need to be 0000004f, get 0000004f  
~~~ OK: end of cycle    2 reg 07 need to be 00000003, get 00000003  
~~~ OK: end of cycle    3 reg 1c need to be 0000004c, get 0000004c  
~~~ OK: end of cycle    4 reg 1c need to be 00000003, get 00000003  
~~~ OK: end of cycle    5 reg 1c need to be 00000278, get 00000278  
~~~ OK: end of cycle    6 reg 1c need to be 00000000, get 00000000  
~~~ OK: end of cycle    7 reg 1c need to be 00000001, get 00000001  
~~~ OK: end of cycle    8 reg 1c need to be 0000004c, get 0000004c  
~~~ OK: end of cycle    9 reg 1c need to be 00000009, get 00000009  
~~~ OK: end of cycle    10 reg 1c need to be 0000004f, get 0000004f  
~~~ OK: end of cycle    11 reg 06 need to be ffffffff1, get ffffffff1  
~~~ OK: end of cycle    12 reg 1c need to be ffffffff4, get ffffffff4  
~~~ OK: end of cycle    13 reg 1c need to be ffffffff6, get ffffffff6  
~~~ OK: end of cycle    14 reg 1c need to be 1fffffff6, get 1fffffff6  
~~~ OK: end of cycle    15 reg 1c need to be 00000001, get 00000001  
~~~ OK: end of cycle    16 reg 1c need to be 00000000, get 00000000  
~~~ Begin test case      mem ~~~  
~~~ OK: end of cycle    1 reg 0a need to be 00008000, get 00008000  
~~~ OK: end of cycle    2 reg 0a need to be 00008010, get 00008010

本文最大执行时间: 50秒 本次评测耗时(编译、运行总时间): 0.471秒

评测

8.实验中遇到的问题及解决办法

- pc 早期一直是 0，后来是发现在复位过程中没有给 next_pc 赋初值。
- 跳转指令执行异常，因为在给ALU的输入端赋值时应该使用 pc 而非 next_pc。

9.实验得到的启示

需要注意在给不同的部件赋值时，信号的时序关系已经不同了。

10.意见和建议

无